

## Motor Connections (via L293D Motor Driver)

- **Motor A (Left Motor)**
  - IN1 → Arduino **Digital Pin 6**
  - IN2 → Arduino **Digital Pin 7**
  - OUT1 → **N20 Motor A +**
  - OUT2 → **N20 Motor A -**
- **Motor B (Right Motor)**
  - IN3 → Arduino **Digital Pin 8**
  - IN4 → Arduino **Digital Pin 9**
  - OUT3 → **N20 Motor B +**
  - OUT4 → **N20 Motor B -**

## Power Connections

- **VCC (L293D)** → **5V** on Arduino
- **GND (L293D)** → **GND** on Arduino and the battery
- **Motor Power (L293D)** → **External Battery (7.4V – 12V)**

## Sensor Connections (8 Line Sensor Array)

- **SENSOR1** → **A0** (Arduino Analog Pin)
- **SENSOR2** → **A1** (Arduino Analog Pin)
- **SENSOR3** → **A2** (Arduino Analog Pin)
- **SENSOR4** → **A3** (Arduino Analog Pin)
- **SENSOR5** → **A4** (Arduino Analog Pin)
- **SENSOR6** → **A5** (Arduino Analog Pin)
- **SENSOR7** → **Digital Pin 10** (Arduino)
- **SENSOR8** → **Digital Pin 11** (Arduino)

## Connections Overview:

1. **Motor A (Left Motor):**
  - IN1 → Digital Pin 6
  - IN2 → Digital Pin 7
  - OUT1 → Left Motor + (N20 Motor A +)
  - OUT2 → Left Motor - (N20 Motor A -)
2. **Motor B (Right Motor):**
  - IN3 → Digital Pin 8
  - IN4 → Digital Pin 9
  - OUT3 → Right Motor + (N20 Motor B +)
  - OUT4 → Right Motor - (N20 Motor B -)
3. **Line Sensors:**
  - SENSOR1 → A0
  - SENSOR2 → A1
  - SENSOR3 → A2

- SENSOR4 → A3
- SENSOR5 → A4
- SENSOR6 → A5
- SENSOR7 → Digital Pin 10
- SENSOR8 → Digital Pin 11

**4. Power:**

- VCC (L293D) → 5V on Arduino
- GND (L293D) → GND on Arduino and Battery
- Motor Power (L293D) → External Battery (7.4V–12V)